

0

1

2

3

4

A

Lab Challenge #3

V1 = 24VDC

L1 (HOT)

L2 Neutral

B

F1
5_AMP

C

S2

Key = Space

S3

Key = Space

CR1

CR

D

Contact3

CR1

Contact4

CR2

CR2

CR

E

Contact1

CR1

White



LAMP

F

Contact2

CR1

Red



LAMP

G